

Lab 3

Kirchhoff's Current Law

A. Background

In 1845, a German physicist Gustav Robert Kirchhoff stated two rules regarding the behavior of electrical circuits. The first rule, known as Kirchhoff's Current Law (KCL), is about the currents entering and exiting a node (junction). KCL states that “sum of all currents entering and the sum of all currents leaving a node must be equal”.

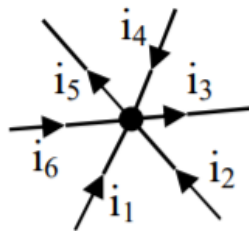


Fig. 3.1.

Consider the above node given in Fig. 3.1.

Currents entering the node = $\{i_1, i_2, i_4, i_6\}$

Currents leaving the node = $\{i_3, i_5\}$

Therefore, KCL states that:

$$i_1 + i_2 + i_4 + i_6 = i_3 + i_5$$

Current Divider:

Consider the circuitry given in Fig. 3.2.

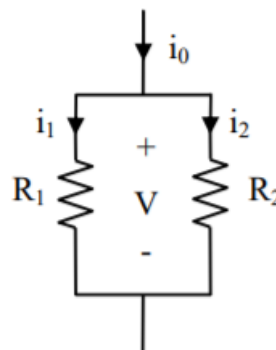


Fig. 3.2.

For the upper node, i_0 is the entering current and i_1 and i_2 are the leaving currents. Then,

$$i_0 = i_1 + i_2$$

The voltage drops over the resistors are equal, then,

$$R_1 i_1 = R_2 i_2$$

Solving the above two equations simultaneously, the branch currents i_1 and i_2 can be expressed in terms of the incoming total current i_0 as:

$$i_1 = \frac{R_2}{R_1 + R_2} i_0 \quad i_2 = \frac{R_1}{R_1 + R_2} i_0 \quad \&$$

B. Experimental Work

B.1. Current Divider & KCL

Consider the circuit given in Fig. 3.3.

- 1) Use OrCAD/PSpice to find the currents i_0 , i_1 , i_2 , i_3 and i_4 by performing bias point analysis.
- 2) Set up the given circuit on a breadboard and measure the currents i_0 , i_1 , i_2 , i_3 and i_4 .
 $i_0 = 0,00098\text{mA}$
 $i_1 = 0,00041\text{mA}$
 $i_2 = 0,00055\text{mA}$
 $i_3 = 0,00023\text{mA}$
 $i_4 = 0,00082\text{mA}$
- 3) Express the currents i_1 and i_2 in terms of the current i_0 , using current division rule. Similarly express the currents i_3 and i_4 in terms of the current i_0 , using the current division rule. Calculate the currents i_0 , i_1 , i_2 , i_3 and i_4 , and verify KCL at all nodes.



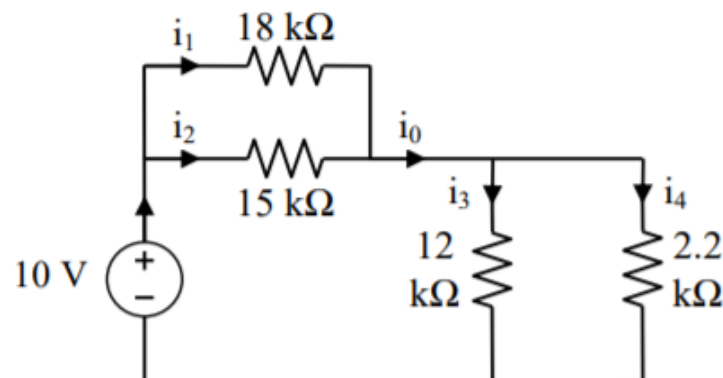


Fig. 3.3. Current Divider Circuit

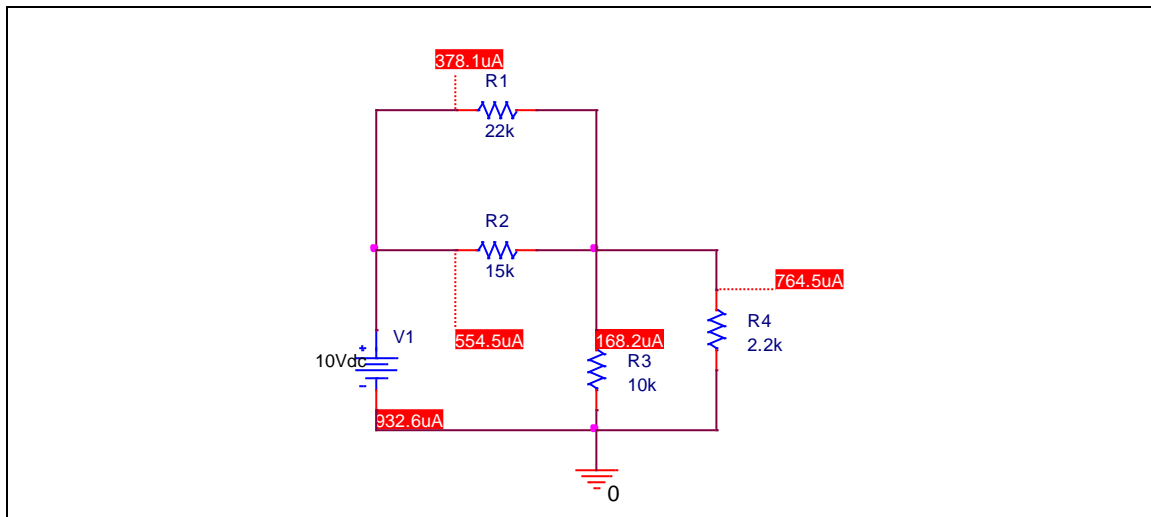i. *Circuit Schematic & Simulation Output (i_0 , i_1 , i_2 , i_3 and i_4)*



ii. *Hand Calculations (Q3)*

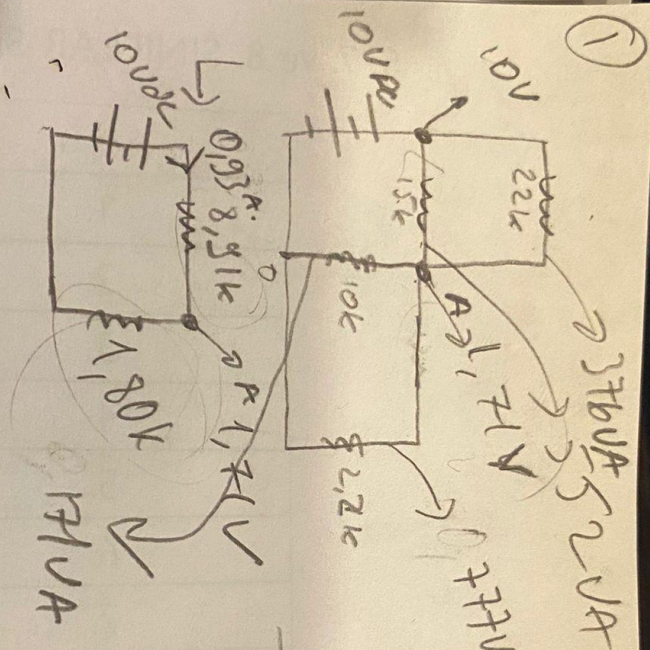

$$I = \frac{V}{R}$$

$$\frac{1.71V}{22k} + \frac{1}{15k} =$$


$$(15) (12)$$

$$\frac{1.8 + 22}{330} = \frac{37}{330} = 8.91k\Omega$$

$$\frac{1}{10k} + \frac{1}{2.2k} = \frac{2.2 + 10}{22k} = \frac{37}{22k}$$

$$(22) (110)$$
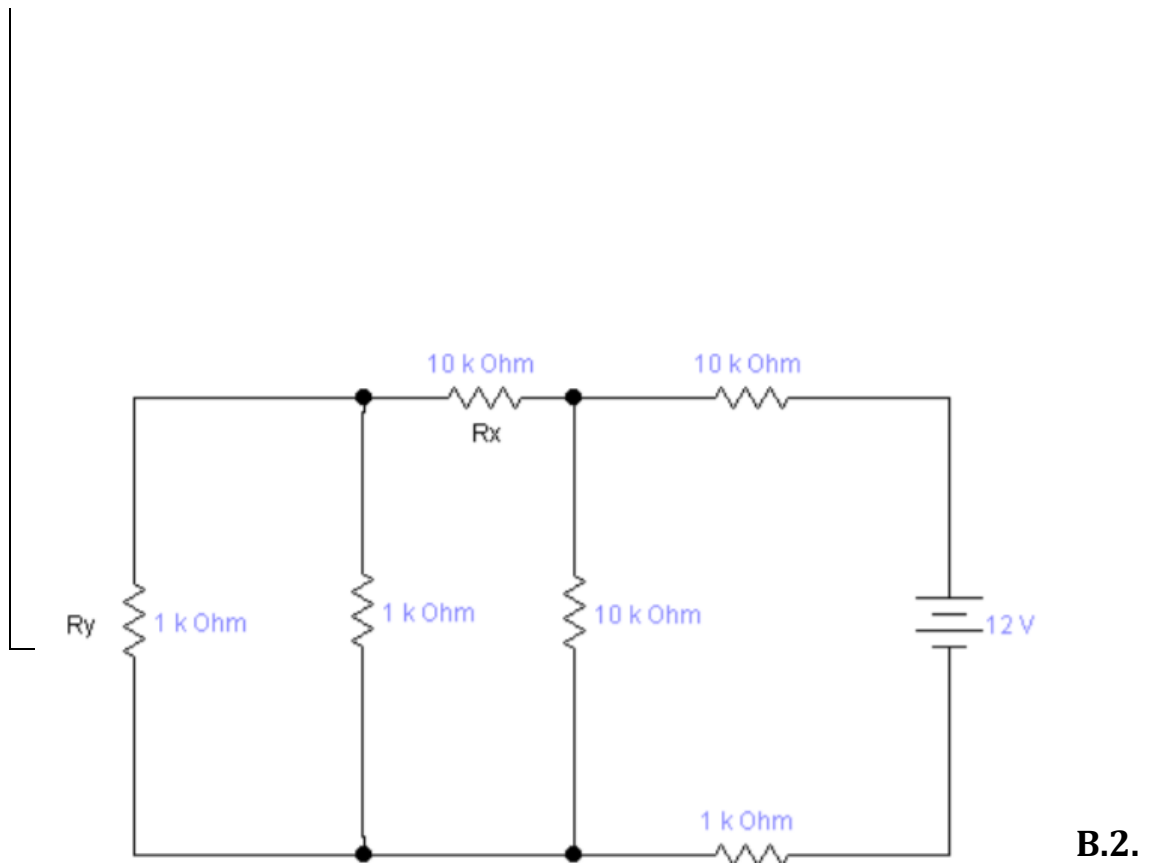
$$\frac{10}{10.72k} = 0.93A \quad 1.80k$$




Equivalent Resistance

Consider the circuit given in Fig. 3.4.

- 1) Simulate the circuit in OrCAD/PSpice and find the current flowing through the 12V voltage source.
- 2) Calculate the equivalent resistance seen from the terminals of voltage source.
- 3) How can you measure the equivalent resistor experimentally? What is the measured equivalent resistor?

Fig. 3.4. A simple resistive circuit

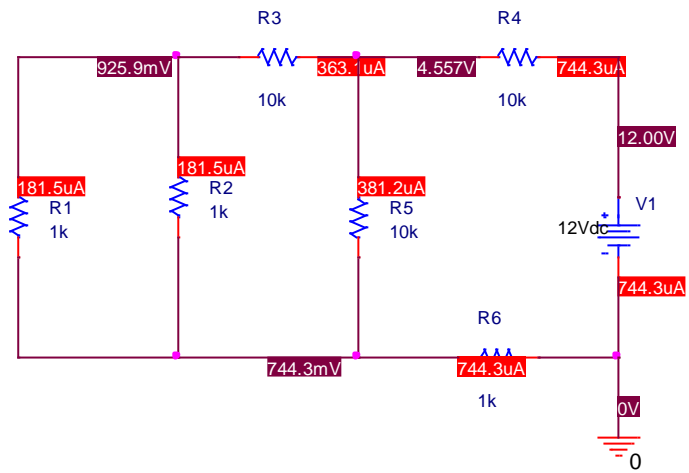
iii. *Circuit Schematic & Simulation Output (The current flowing through 12V voltage source)*



- iv. *Hand Calculations (Calculate the equivalent resistance seen from the terminals of voltage source) 16*

$$\frac{10}{10,75k} \left[0,93A \right] 1,80k$$

②

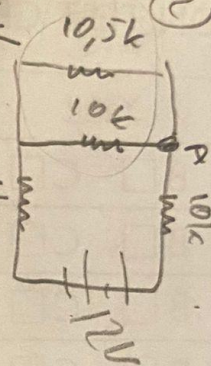

$$\frac{1}{10,5} + \frac{1}{10} = \frac{20,5}{105} = 5,12$$

$$16,12 \text{ Re}$$

$$\frac{12}{16,12} = 0,74A$$

$$12 - 7,4 = 4,6V$$

$$0,74 \cdot 10 = 7,4$$

$$20,5 + = 0,74$$

$$\frac{20,5}{10} = 2,05$$

$$(10)$$

$$12$$

$$- 20,5 = - 20,5$$

$$- 20,5$$

